

**Sizing and PSPICE simulation of a Mixer**

18/11/2018 – Diego Tuzi – 50435 – [diego.tuzi@studentmail.unicas.it](mailto:diego.tuzi@studentmail.unicas.it)

**POINT 1A and 1B**

Determine the capacitance  $C_{ris}$  in the common emitter amplifier of Fig.1, so as to obtain the resonance frequency of 10.7MHz that is the intermediate frequency of the mixer. Consider that the transformer TX1, which will be used in the experimental circuit, has an inductance of the primary,  $L_{prim}$ , equal to 4.71uH .

Determine the minimum value of resistance  $R_L$  which allows you to obtain a  $Q$  greater than 10 and guarantees a good selectivity of the stage while retaining a bandwidth compatible with the FM signal of interest.

$$\omega_0 = \frac{1}{\sqrt{L_1 \cdot C_{ris}}} \quad , \quad \omega_0 = 2\pi f_0$$

$$C_{ris} = \frac{1}{L_1 (2\pi f_0)^2} \quad , \quad f_0 = 10,7 \text{ MHz} \quad , \quad C_{ris} = 46,97 \text{ pF}$$

For a parallel RLC circuit


$$Q = R_L \sqrt{\frac{C_{ris}}{L_1}} \quad \rightarrow \quad R_L = Q \sqrt{\frac{L_1}{C_{ris}}}$$

$Q > 10$  when  $R_L > 3,17 \text{ k}\Omega$

$$Q = \frac{f_0}{BW} \quad \rightarrow \quad BW \approx 1,07 \text{ MHz}$$

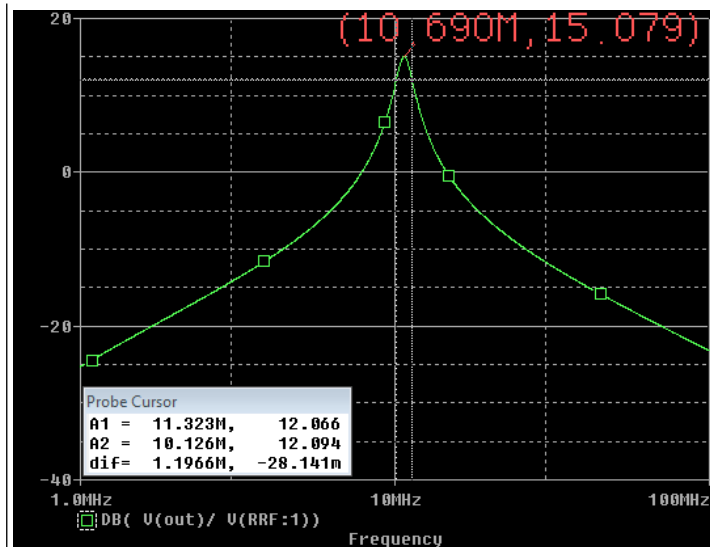**POINT 2B**

Perform the AC analysis to check that the amplifier is tuned to the frequency of interest. Set the AC input generators VRF and VLO to 5mV and 0V, respectively. Determine quality factor  $Q$  and gain  $A$  of the amplifier at the resonance frequency. Verify that it is  $g_m \cdot r_0 // R_L$ .



From simulation

$f_0 = 10,69\text{MHz}$   
 voltage gain ( $A_{db}$ ) = 15,08 dB  
 bandwidth = 1,20 MHz  
 $Q = 8,93$

from theory

$$A_{db} = 20 \log_{10}(g_m (r_0 // R_0))$$

$$A_{db} = 20 \log_{10} \left( g_m \left( \frac{r_0 R_0}{r_0 + R_0} \right) \right) \approx 23,58 \text{ dB}$$

**Sizing and PSPICE simulation of a Mixer**

18/11/2018 – Diego Tuzi – 50435 – [diego.tuzi@studentmail.unicas.it](mailto:diego.tuzi@studentmail.unicas.it)


**POINT 2C**

Perform a transient analysis to verify the correct behavior of the mixer.


In simulation set the parameters as :

- amplitude and frequency of VRF to 10mV and 98MHz, respectively;
- amplitude and frequency of VLO to 500mV and 108.7MHz, respectively;
- initial condition on the capacitor CE to 0.5595V;
- simulation interval to 50  $\mu$ s;
- step ceiling to 0.1ns.

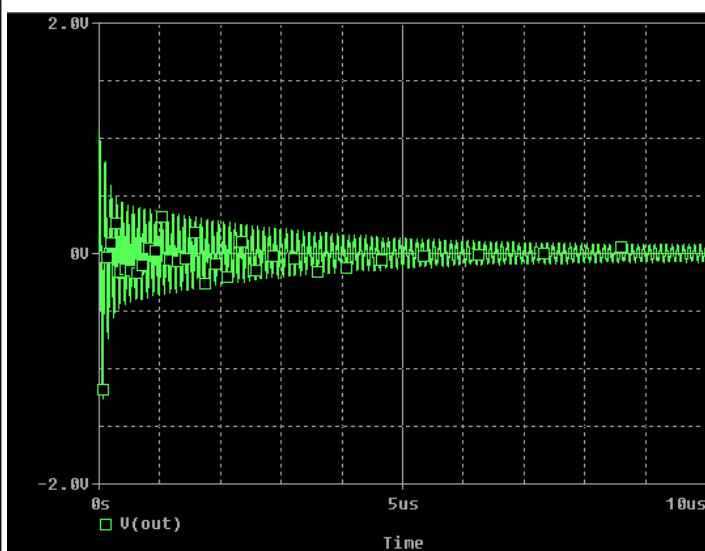Display the signal in the time domain and its FFT. Identify the harmonics and various intermodulation products and, in particular, recognize RF, LO and intermediate frequency components.



Time Domain

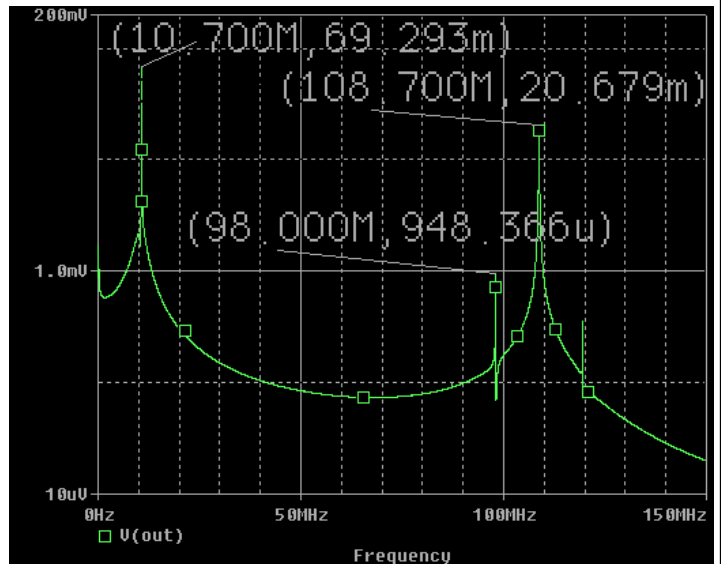

FFT

IF at 10,7 MHz with 69,3mV of amplitude  
 RF at 98 MHz with 948,4uV of amplitude  
 LO at 108,7 MHz with 20,7mV of amplitude

Report on a table the values of the amplitudes and frequencies of the main harmonics up to the 5 th order.

n	+/-	m	f (MHz)	a(mV)
1	-	1	10,70	69,293
1	+	0	98,00	0,948
0	-	1	108,70	20,679
1	-	2	119,40	0,352
1	+	1	206,70	0,369
0	+	2	217,40	5,895
1	-	3	228,10	0,091
2	-	4	238,80	0,002
2	+	1	304,70	0,003
1	+	2	315,40	0,143
0	+	3	326,10	1,819
1	-	4	336,80	0,029
2	+	2	413,40	0,002
1	+	3	424,10	0,052
0	+	4	434,80	0,569
1	-	5	445,50	0,009
2	+	3	522,10	0,001
0	+	5	543,50	0,179
1	+	5	641,50	0,006
2	+	5	739,50	0,001


**Sizing and PSPICE simulation of a Mixer**

18/11/2018 – Diego Tuzi – 50435 – [diego.tuzi@studentmail.unicas.it](mailto:diego.tuzi@studentmail.unicas.it)

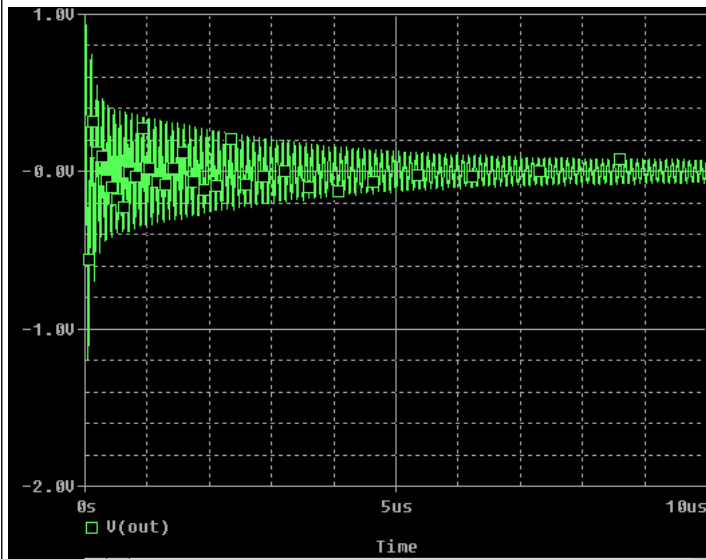
**POINT 2D**

Repeat the procedure referred to in point c for the maximum frequency RF.

Display the signal in the time domain and its FFT. Identify the harmonics and various intermodulation products and, in particular, recognize RF, LO and intermediate frequency components.



Time Domain

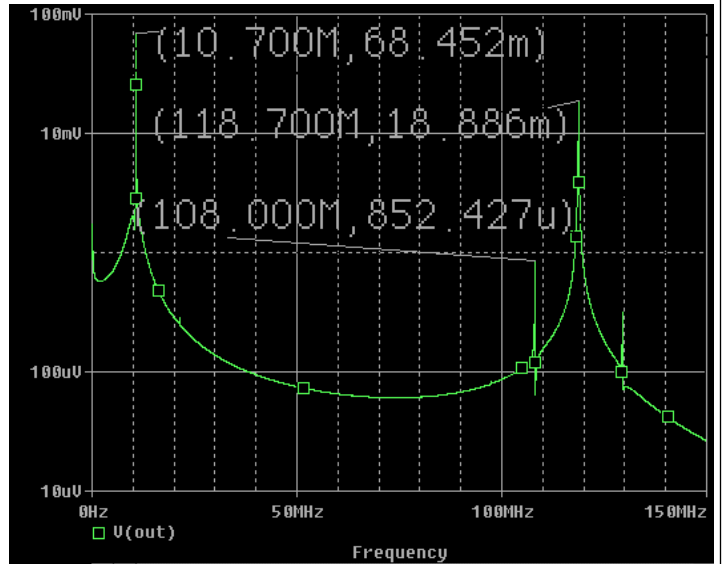

FFT

IF at 10,7 MHz with 68,4mV of amplitude  
 RF at 108 MHz with 852,4uV of amplitude  
 LO at 118,7 MHz with 18,9mV of amplitude

Report on a table the values of the amplitudes and frequencies of the main harmonics up to the 5th order.

n	+/-	m	f	a(mV)
1	-	1	10,70	68,452
1	+	0	108,00	0,852
0	+	1	118,70	18,886
1	-	2	129,40	0,316
2	+	0	216,00	0,014
1	+	1	226,70	0,327
0	+	2	237,40	5,266
1	-	3	248,10	0,082
2	+	1	334,70	0,002
1	+	2	345,40	0,125
0	+	3	356,10	1,602
1	-	4	366,80	0,026
2	+	2	453,40	0,002
1	+	3	464,10	0,045
0	+	4	474,80	0,498
1	-	5	485,50	0,008
2	+	3	572,10	0,001
1	+	4	582,80	0,015
0	+	5	593,50	0,153
1	+	5	701,50	0,005
2	+	5	809,50	0,001


**Sizing and PSPICE simulation of a Mixer**

18/11/2018 – Diego Tuzi – 50435 – [diego.tuzi@studentmail.unicas.it](mailto:diego.tuzi@studentmail.unicas.it)

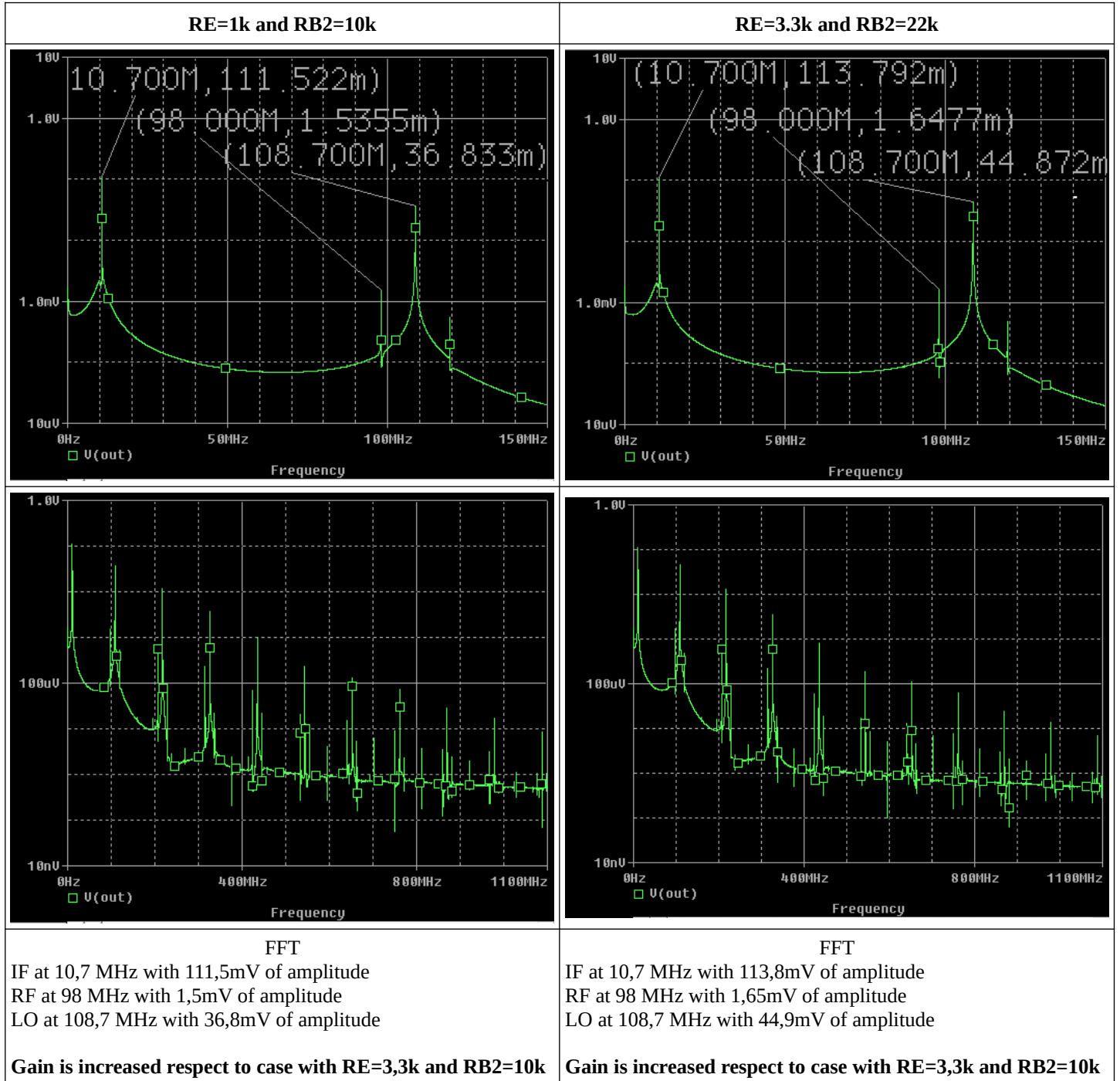**POINT 2E**

Study the effect of variation of the biasing point on the frequency response of the mixer. For this purpose, using the parameters indicated in point c, analyze the two following cases:

- $RE=1k$  and  $RB2=10k$ ;
- $RE=3.3k$  and  $RB2=22k$ .



**Sizing and PSPICE simulation of a Mixer**

18/11/2018 – Diego Tuzi – 50435 – [diego.tuzi@studentmail.unicas.it](mailto:diego.tuzi@studentmail.unicas.it)

**POINT 2F**


The mixer circuit must be connected with a load adapted to 50 Ohm. For this purpose design a two element matching network as shown in Fig. 2. For computing  $L_{Adatt}$  and  $C_{Adatt}$  refer to the link used in the previous exercises. Consider the value of  $R_L$  found in point 1.a at the input side and 50 at the output one.

Source Resistance: 3170 Source Reactance: 0

Load Resistance: 50 Load Reactance: 0

Desired Q:  Frequency: 10.7e6


**LOWPASS Hi-Low MATCHING NETWORK**

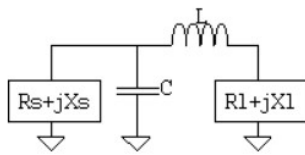


L Value: 5874.875 nH

C Value: 37.06545 pF


Q Value: 7.899367

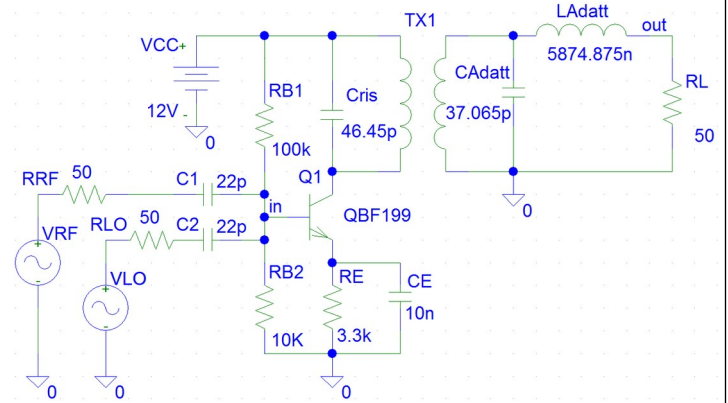

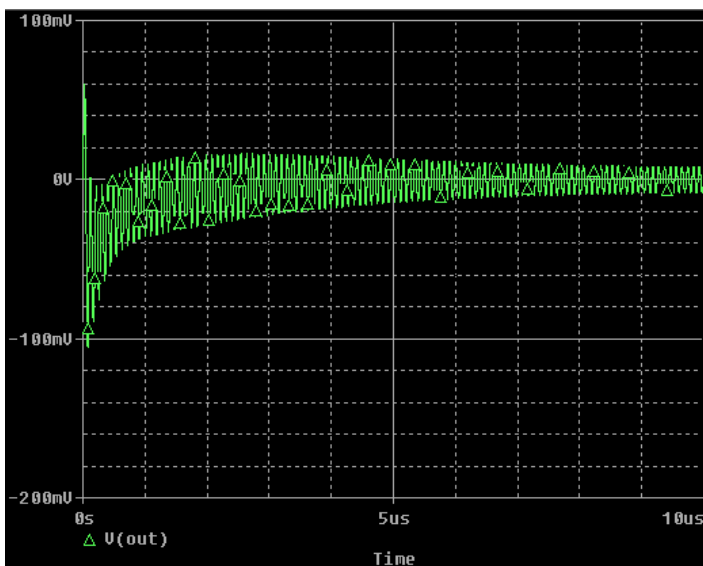Repeat the analysis requested in point 2.c to verify the correct operations of the mixer in the whole range of frequency.



Time Domain

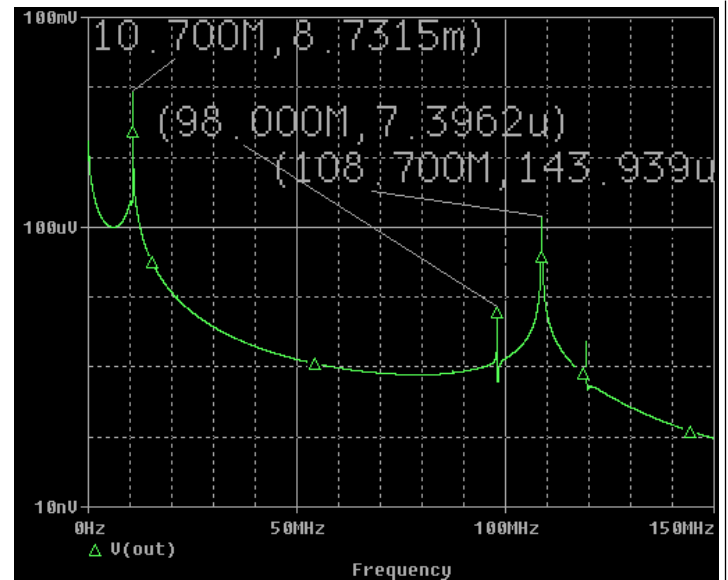

FFT

IF at 10,7 MHz with 8,7mV of amplitude  
 RF at 98 MHz with 7,4uV of amplitude  
 LO at 108,7 MHz with 143,9uV of amplitude